

University of Illinois at Urbana-Champaign
Dept. of Electrical and Computer Engineering

ECE 120: Introduction to Computing

Storing a Bit:
the Gated D Latch

ECE 120: Introduction to Computing

© 2016-2017 Steven S. Lumetta. All rights reserved.

slide 1

Everything So Far Has Been Combinational Logic

So far, we have talked only about
combinational logic.

Combinational logic allows us to solve the
following type of problem:

- given a set of bits as input,
- how can we combine them to produce other
sets of bits (Boolean expressions)?

But where do the input bits come from?

ECE 120: Introduction to Computing

© 2016-2017 Steven S. Lumetta. All rights reserved.

slide 2

Now Let's Look at Sequential Logic

Today, we will start to look at
sequential logic.

Sequential logic

- **stores bits as state**, and
- its **behavior depends on the state**
(the values of the stored bits),
- just like the behavior of a C program can
depend on the current values of variables.

ECE 120: Introduction to Computing

© 2016-2017 Steven S. Lumetta. All rights reserved.

slide 3

A Dual "Inverter" Loop Serves a Specific Purpose

**What is a 1-input NAND
gate?**


An inverter / NOT.

**Remember the gate
structures?**

What does the circuit here do?

It has no inputs!

How can we analyze it?

 

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 4

Start Solving by Picking a Value for Some Variable

First, **write a truth table**.

Then **pick a value**.


Say **$Q = 0$** .

Which implies what about P ?

$P = 1$.

Which implies what about Q ?


$Q = 0$ (be sure to check!).

 

Q	P
0	1

Trace Logic Values to Find Stable States

 We say that this state (**$Q = 0$** , and **$P = 1$** , as shown in the truth table) is **stable** because the values do not continue to change forever.



What if we instead pick **$Q = 1$** ?

In that case, what is P ?

And what does $P = 0$ imply for Q ?

Again, be sure to check stability.


Q	P
0	1
1	0

The Dual-Inverter Loop Stores One Bit

We say that this circuit is **bistable** because it has **two stable states** (bi- = two).

Bits on a chip are typically stored using this kind of dual-inverter loop.

But ... **how do we set a value?**

 

Q	P
0	1
1	0

Use an Extra Input to Set the Bit Q

Let's add an input.

We will call it **S'** .

What happens when S' is 1?


The new input has no effect!

(green is the previous truth table)

What if $S' = 0$?

$Q = 1$! And $P = 0$.

So S' Sets the bit Q to 1.

 

S'	Q	P
0	1	0
1	0	1
1	1	0

Active Low Inputs are Named with “Bar” (NOT)

Why did we call the input S' ?

(Call it “S bar,” by the way.)

The action induced by S' ,

- to **S(et) the bit Q**,
- occurs when $S' = 0$ (S' is low).

We say that the input S' is **active low**.


And we name it S' instead of \bar{S} to indicate how the input should be used.

What About Resetting Q to 0?

So we can set $Q = 1$.

But ... what if we want $Q = 0$?

 Keep flipping the power on and off until we get lucky?
(Maybe not.)



S'	Q	P
0	1	0
1	1	0
1	0	1

Any ideas?

Use an Extra Input to Reset the Bit Q

Another input? Sure.

We will call it R' .


What happens when R' is 1?

The new input has no effect!
(green is the previous table)

What if $R' = 0$ and $S' = 1$?

$P = 1$! And $Q = 0$.

So R' Resets the bit Q to 0.

 

R'	S'	Q	P
0	1	0	1
1	0	1	0
1	1	0	1
1	1	1	0


An R' - S' Latch Consists of Two NAND Gates

This circuit has a name!

It's an **R' - S' latch**
("R bar, S bar latch").

Store a **1 bit** by lowering S' to 0.

Store a **0 bit** by lowering R' to 0'.

 

R'	S'	Q	P
0	1	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Avoid Setting Both S' and R' to 0 Simultaneously


What if we set both S' and R' to 0 at the same time?

$Q = 1$ and $P = 1$.

But when we raise the inputs, we may leave the stored bit in either state.

Or, worse, the loop may not settle into digital voltages (**metastable**).

Do NOT lower both at once!

 


ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 13

 Extra Gates Prevent the Forbidden Input Combination



We can add a couple more NAND gates to prevent setting both S' and R' to 0.

Let's check the truth table.

So Q stores D ...


D	R'	S'	Q	P
0	0	1	0	1
1	1	0	1	0

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 14

 We Can Simplify the Design to Copy D to Q



There's an easier way to implement such a circuit, though...

So Q stores D ...


D	R'	S'	Q	P
0	0	1	0	1
1	1	0	1	0

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 15

Extra Inputs Control Copying of D to Q

 

Let's add more inputs to the new gates, too.

Now our design only copies D to Q when $WE = 1$.

WE	D	R'	S'	Q	P
1	0	0	1	0	1
1	1	1	0	1	0

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 16

The Circuit Can Also Store a Bit


What happens when WE = 0?

The circuit stores the last bit from **D** (same truth table as before!).

This circuit is called a **gated D latch**.

WE	D	R'	S'	Q	P
1	0	0	1	0	1
1	1	1	0	1	0
0	x	1	1	0	1
0	x	1	1	1	0

This Design is Called a Gated D Latch

 

Symbolically, a **gated D latch** is drawn as shown here.

Notice that **P** has been replaced by **Q'**, since they are always complements of one another.

