

University of Illinois at Urbana-Champaign
Dept. of Electrical and Computer Engineering

ECE 120: Introduction to Computing

Checking for Upper-Case Characters

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 1

Task: Checking for an Upper-Case Letter

Let's design logic to check whether an **ASCII** character is an upper-case letter.

In **ASCII**, 'A' is **1000001** (0x41),
and 'Z' is **1011010** (0x5A).

Let's say that the **ASCII** character
is in $C = C_6C_5C_4C_3C_2C_1C_0$.

**How can we check whether
C represents an upper-case letter?**

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 2

We Will Need a BIG Truth Table!

Should we write a truth table for U(C) ?	C_6	C_5	C_4	C_3	C_2	C_1	C_0	U(C)
	0	0	0	0	0	0	0	0
	0	0	0	0	0	0	1	0
	0	0	0	0	0	1	0	0
	0	0	0	0	0	1	1	0
Can we skip to the ones that matter?	0	0	0	0	1	0	0	0
	0	0	0	0	1	0	1	0
	0	0	0	0	1	1	0	0
	0	0	0	0	1	1	1	0

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 3

Let's Break the Truth Table into Eight Pieces

Can we **break the truth table into pieces**?

For example, let's break the truth table

- into eight truth tables
- of 16 rows each.

Each piece represents one value of $C_6C_5C_4$.

We can solve each piece with a
K-map on $C_3C_2C_1C_0$.

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 4

Some Functions are Quite Simple

Or maybe we don't need a K-map for some.

Remember that 'A' is **1000001** (0x41),
and 'Z' is **1011010** (0x5A).

Think about the table for $C_6C_5C_4 = 000$?*

What is the function of $C_3C_2C_1C_0$? **0**

(In other words, no **ASCII** character with
 $C_6C_5C_4 = 000$ is an upper-case letter.)

* This notation means $C_6 = 0$ AND $C_5 = 0$ AND $C_4 = 0$.

Only Two of Our Functions are Not the 0 Function

For reference: 'A' is **1000001** (0x41), and
'Z' is **1011010** (0x5A).

Which of our eight functions are
not the 0 function?

$C_6C_5C_4 = 100$ Let's call the function T_4 .

$C_6C_5C_4 = 101$ Let's call the function T_5 .

Let's solve K-maps for these two.

Solve T_4 Using a Single Loop

Let's solve T_4 . Should we use SOP or POS?

T_4 is a maxterm!

$$T_4 = (C_3 + C_2 + C_1 + C_0)$$

		C_3C_2			
		00	01	11	10
C_1C_0	00	0	1	1	1
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1

Solve T_5 as a POS Expression

Let's solve T_5 . POS is better again.

What are the loops?
for SOP?

$$(C_3' + C_2')$$

$$(C_3' + C_1' + C_0')$$

$$\text{So } T_5 = (C_3' + C_2') \cdot (C_3' + C_1' + C_0')$$

		C_3C_2			
		00	01	11	10
C_1C_0	00	1	1	0	1
	01	1	1	0	1
	11	1	1	0	0
	10	1	1	0	1

Combine T_4 and T_5 to find $U(C)$

How do we combine T_4 and T_5 to find the full upper-case checker function $U(C)$?

Remember:

- T_4 applies when $C_6C_5C_4 = 100$, and
- T_5 applies when $C_6C_5C_4 = 101$.

So ...?

- AND T_4 with $C_6C_5'C_4'$,
- AND T_5 with $C_6C_5'C_4$, and
- OR the results together.

A Good Solution, But Maybe We Can Do Less Work?

$$\text{So } U(C) = C_6C_5'C_4'(C_3 + C_2 + C_1 + C_0) + C_6C_5'C_4(C_3' + C_2')(C_3' + C_1' + C_0')$$

That's a pretty small and fast solution.

But we still had to do a fair bit of work.


Is there an easier way?

Consider the following: to check for an upper-case letter, we need to know whether

$$C \geq 1000001 \text{ AND } C \leq 1011010$$

Use Two Comparators to Calculate $U(C)$


What about this approach?

 

Or Use Two Adders to Calculate $U(C)$

Or this approach?

 Note that the adders are performing subtractions.



Inefficient, But Simple to Design

Quite large and slow compared with our first solution?

Consider two arguments:

1. CAD tools can optimize away much of the extra overhead.
2. Software executing on data center servers around the world executes the adder design even less efficiently, but it's constantly in use on hundreds of thousands of machines.