

University of Illinois at Urbana-Champaign  
Dept. of Electrical and Computer Engineering

## ECE 120: Introduction to Computing

### Multiplexers (MUXes)

ECE 120: Introduction to Computing

© 2016-2017 Steven S. Lumetta. All rights reserved.

slide 1

## Task: Checking for a Lower-Case Letter

What if we also need logic to check whether an **ASCII** character is a lower-case letter.

In **ASCII**, 'a' is **1100001** (0x61),  
and 'z' is **1111010** (0x7A).

Recall that 'A' is **1000001** (0x41),  
and 'Z' is **1011010** (0x5A).

**Can we reuse our solutions  
for upper-case letters?**

**Of course we can!**

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 2

## Change $C_5$ to $C_5$ to Obtain $L(C)$ from $U(C)$

Let's again say that the **ASCII** character  
is in  $C = C_6C_5C_4C_3C_2C_1C_0$ .

By breaking up the truth table, we obtained

$$U(C) = C_6C_5C_4(C_3 + C_2 + C_1 + C_0) + C_6C_5C_4(C_3 + C_2)(C_3 + C_1 + C_0)$$

But lower-case characters are only different  
from upper-case in  $C_5$ , which is 1 instead of 0.

$$L(C) = C_6C_5C_4(C_3 + C_2 + C_1 + C_0) + C_6C_5C_4(C_3 + C_2)(C_3 + C_1 + C_0)$$


ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 3

## Change Comparator Input to Calculate $L(C)$

Or just change the comparators' inputs.

 

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 4

## Want Logic to Choose Between Two Signals

What if we want one design to check for either upper-case or lower-case letters?

In a few examples,

- we added a control signal  $S$
- to select between functions.

Can we design logic

- that uses a control signal  $S$  to select
- between two arbitrary signals,  $D_1$  (when  $S = 1$ ) and  $D_0$  (when  $S = 0$ )?

## Truth Tables for a 2-to-1 Multiplexer

A full truth table for such logic appears to the right.

But we could shorten it as shown below...

$S$	$D_1$	$D_0$	$Q$
0	x	0	0
0	x	1	1
1	0	x	0
1	1	x	1

Unselected inputs do not matter (marked with "x").

$S$	$D_1$	$D_0$	$Q$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

## We Normally Use the Most Compact Truth Table

In this case, we can even write outputs in terms of other inputs, as shown here.

$S$	$D_1$	$D_0$	$Q$
0	x	0	0
0	x	1	1
1	0	x	0
1	1	x	1

Unselected inputs do not matter (marked with "x").

$S$	$Q$
0	$D_0$
1	$D_1$

## Expression for a 2-to-1 Multiplexer

Let's solve with a K-map.

$$Q = S'D_0 + SD_1$$

		$D_1D_0$			
		00	01	11	10
$S$	0	0	1	1	0
	1	0	0	1	1

$S$	$D_1$	$D_0$	$Q$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

## Expression for a 2-to-1 Multiplexer

But  $Q$  just selects  $D_0$  or  $D_1$  (as desired)!

$$Q = S'D_0 + SD_1$$


S	Q
0	$D_0$
1	$D_1$

Could we have just written this expression using the table to the right?

$Q$  is  $D_0$  when  $S = 0$ , and  $D_1$  when  $S = 1$ ...
 
## Implementation and Symbolic Form of a 2-to-1 Mux

The circuit below shows a **2-to-1 mux (multiplexer)**, for which the symbolic form appears to the right.




## Selecting from More than Two Expressions

What if we want to select between four expressions,  $D_3$ ,  $D_2$ ,  $D_1$ , and  $D_0$ ?

One answer is to use muxes hierarchically:

 - start by using one 2-to-1 mux (signal  $S_1$ )
- to decide between  $D_3$  or  $D_2$  and  $D_1$  or  $D_0$ .




## For the Second Level, Use More Muxes

But how do we deliver two expressions to each mux input?

Use more muxes (both controlled by  $S_0$ )!

 
Notice that  $S_1S_0$  then allows us to choose from four expressions.



## AND Gates Represent Minterms ANDed with Data Inputs

For something as common as a mux, we typically build directly from gates.

Notice that **each AND gate produces a minterm of  $S_1, S_0$**  ANDed with the corresponding  $D_i$ .

 

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.


slide 13

## A $2^N$ -to-1 Mux Requires N Select Bits

The diagram to the right shows the **symbolic form of a 4-to-1 mux**.

We can, of course, further extend this idea to build 8-to-1 muxes, 16-to-1 muxes, and so forth.

When selecting amongst  $P = 2^N$  inputs  $D_{P-1} \dots D_0$  we need  $N$  bits of select input,  $S_{N-1} \dots S_0$ .

 

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 14

## Can Use Sets of Muxes to Select Amongst Groups of Bits

We can also generalize the idea of multiplexers by

- using a common control signal
- to select between groups of inputs.

Generally,

- **an N-to-M multiplexer**
- **represents M separate (N/M)-to-1 muxes**
- each with  $\log_2(N/M)$  select bit inputs
- (typically  $N/M = 2^K$  for some integer  $K$ ).

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 15

## Example of a Set of Muxes with Common Select Input

For example, recall the design of the **N-bit** adder and subtractor.

We could have used a **2N-to-N** mux

- to choose between  $B_i$  and  $B_i'$  for the adder's  $B$  input
- based on a common (one-bit) control signal  $S$ .

(Previously, we used the nature of the mux' data inputs,  $B_i$  versus  $B_i'$ , to simplify each mux' logic to an XOR gate.)

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 16

## Another Design Problem: Checking Four Types of ASCII

Now think again about our **ASCII** checker.

Say that we want four kinds of comparison:

- control characters (0x00 to 0x1F),
- lower-case letters (0x41 to 0x5A),
- upper-case letters (0x61 to 0x7A), and
- digits (0x30 to 0x39).

**How can we design logic to check for any of the four types?**

## The Answer? Use Muxes! Two 28-to-7 Muxes

