

University of Illinois at Urbana-Champaign
Dept. of Electrical and Computer Engineering

ECE 120: Introduction to Computing

Logic Gates

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 1


Today: How Can We Build Gates?

3. Functions on bits (Boolean operators, gates)

4. Implementation?

2. Representations
based on bits

1. Two voltage levels \rightarrow 1 bit

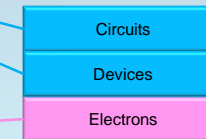

How can we build gates?

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 2

But First: Check Out My New Invention!

Last night I had a great idea.

I call it a **“torch.”**

At night, you can **point it at things.**


And **they will be lit up.**

Anything!

Your car or bike.

Your door lock.

A friend.

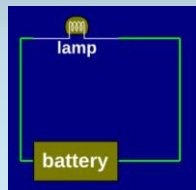

What do you think?

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 3

You Think I Should Do What?


Like this?

I think **people already make those.**

The switch is **controlled by your thumb.**

They call it a **flashlight.**

I won't be able to patent it.

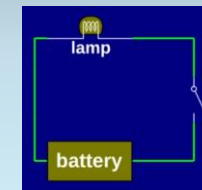

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 4

Don't Worry: Here's Another Idea

So, you like switches?
 Let's put a bunch of switches together.
 Each controlled by ~~our~~ your thumbs.
 When we want **to change a bit**,
 we will just **flip a switch**!
 We'll call it a **hand-operated computer**!
 We'll need about **2,000,000,000** switches.
 What do you think?

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 5

Still Don't Like It? One Last Try...

What if we develop a **voltage-controlled switch**?
 Then **one switch**
 ◦ can **control another switch**,
 ◦ which can **control a third switch**,
 ◦ **and so on**!
 Instead of using **your thumbs**, we can
build circuits with 2,000,000,000 switches!
 Now THAT's a really cool idea!

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 6

Let's Take a Bragging Break

John Bardeen, 1908-1991
 1947: **invented transistor** at Bell Labs
 with Shockley & Brattain
 1951: joined **Illinois ECE faculty**
 (and Physics)
 1956: **Nobel Prize, Physics**
 1972: second **Nobel Prize, Physics**, for
 Bardeen-Cooper-Schrieffer
(BCS) theory of superconductivity

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 7

Bardeen's First Ph.D. Student (1954)

Nick Holonyak, Jr., 1928-
 1962: invented **visible light LED** at GE
 1963: joined **Illinois ECE faculty**
 (also invented laser diodes for **CDs/DVDs**,
dimmer switches, and more)
 1973: **National Academy of Engineering**
 2003: **National Medal of Technology**
 2008: **National Inventors Hall of Fame**
 (among many other awards)

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 8

Holonyak's First(?) Ph.D. Student (1967)

Greg Stillman, 1936-1999

1975: joined **Illinois ECE faculty**

invented **avalanche photodiodes**
(for amplifying small photon sources),
among many other things

1985: **National Academy of Engineering**

1985-1987: **Founding Director of MNTL**
(the Micro- and Nano-Technology Lab)

Stillman's First Ph.D. Student (1979)

Milton Feng, 1950-

1991: joined **Illinois ECE faculty**

2003: invented **Terahertz transistors**

Jan 2004: invented **light-emitting transistor** (with Nick!)

Nov 2004: invented **transistor laser**
(also with Nick!)

2016: just retired...

But Not Just Faculty!

Jack Kilby, 1923-2005

1947: **BSEE from Illinois**

1958-59: invented **integrated circuit** at TI

(also invented the **thermal printer**
and the **handheld calculator**)

1967: **National Academy of Engineering**

2000: **Nobel Prize, Physics**

(See why we expect a lot of you?)

Digital Electronics is Based on MOSFETs

Digital electronics today uses MOSFETs.

- the material: Metal-Oxide Semiconductors
- the mechanism: Field-Effect Transistors
(electric field/voltage-controlled)

There are two kinds, named
after the charge carrier,

- **n**(egative)-**t**ype, and
- **p**(ositive)-**t**ype,

drawn as shown here.




n-type is On With Positive Gate to Source/Drain Voltage

An **n-type MOSFET**

- turns **on** (switch is **closed**, allowing current to flow)
- if the **voltage from gate** (left terminal) **to other terminals exceeds a threshold**

If the voltage is smaller, the transistor is **off** (the switch is **open**).

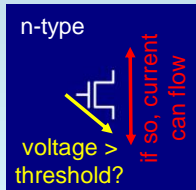

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 13

Our Voltages Will Be Binary

We need two voltages:

- **0V**, a ground (this is the binary 0 value)
- **V_{dd}**, around **1.5V**, high voltage* (this is the binary 1 value)

*Used to be 5V, but has been decreasing for decades. The rate of decrease is now slowing down.

ECE 120: Introduction to Computing


© 2016 Steven S. Lumetta. All rights reserved.

slide 14

Use Binary Voltages to Control n-Type MOSFETs

n-type only turns on when gate voltage is high (**V_{dd}**).

An **n-type** can pull one terminal down to **0V** with the other terminal.

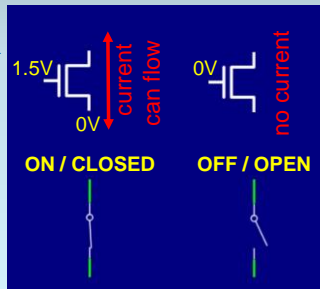

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.


slide 15

p-type is On With Negative Gate to Source/Drain Voltage

A **p-type MOSFET**

- turns **on** (switch is **closed**, allowing current to flow)
- if the **voltage from other terminals to the gate** (left terminal) **exceeds a threshold**

If the voltage is smaller, the transistor is **off** (the switch is **open**).

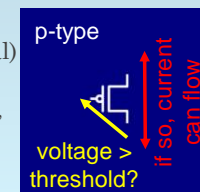

ECE 120: Introduction to Computing


© 2016 Steven S. Lumetta. All rights reserved.

slide 16

Use Binary Voltages to Control p-Type MOSFETs

p-type only turns on when gate voltage is low (0V).

A **p-type** can pull one terminal up to V_{dd} with the other terminal.

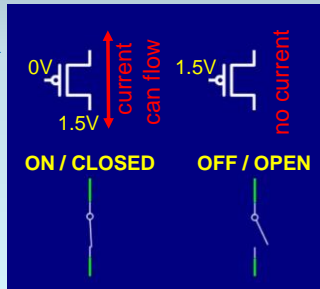

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 17

The Drawings Help You Remember How They Work

Notice the use of the inverter bubble on the **p-type**.

Use it to help you remember:

- **p-type turns on with low voltage** (0V, or binary 0).
- **n-type turns on with high voltage** (V_{dd} , or binary 1).

The names may not be so helpful (again, they refer to charge carriers).



ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 18

Gates are Based on Complementary MOS (CMOS)

So how do we build gates?

Gates use complementary structures of **p-type** and **n-type MOSFETs**.

Each gate uses an equal number of each type.

For that reason, we say that

- most **digital systems are based on CMOS**,
- or Complementary MOS.

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 19


What Does This Gate Do? (when A=0V)

Here is the simplest gate.

What does it do?

Let's write a truth table!

A	Q
0V	1.5V
1.5V	

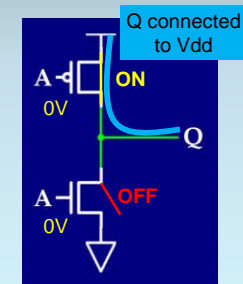

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 20


What Does This Gate Do? (when A=1.5V)

Here is the simplest gate.

What does it do?

Let's write a truth table!

A	Q
0V	1.5V
1.5V	0V

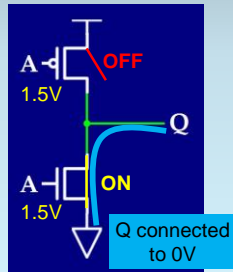

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 21


It's a NOT Gate!

Now convert the truth table from voltages to binary.

It's a NOT gate!

A \neg Q

A	Q
(0) 0V	1.5V (1)
(1) 1.5V	0V (0)

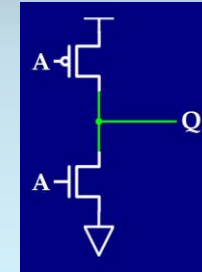

ECE 120: Introduction to Computing


© 2016 Steven S. Lumetta. All rights reserved.

slide 22

Let's Analyze Another Structure

What about this structure?

A	B	Q
0	0	1
0	1	
1	0	
1	1	

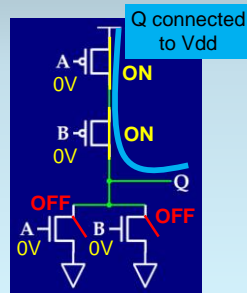

ECE 120: Introduction to Computing


© 2016 Steven S. Lumetta. All rights reserved.

slide 23

Next, Assume A = 0 and B = 1

The A value is the same, so we leave the markings.

A	B	Q
0	0	1
0	1	0
1	0	
1	1	

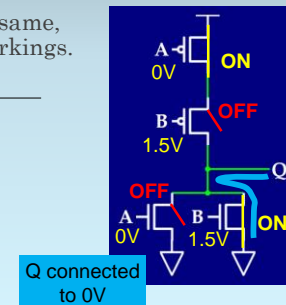

ECE 120: Introduction to Computing


© 2016 Steven S. Lumetta. All rights reserved.

slide 24

Next, Assume A = 1 and B = 1 (BOTTOM LINE!)

The B value is the same, so we leave the markings.

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

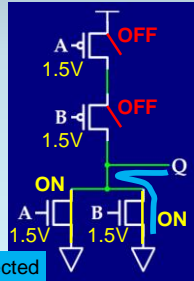

Q connected to 0V

ECE 120: Introduction to Computing


© 2016 Steven S. Lumetta. All rights reserved.

slide 25

Finally, Assume A = 1 and B = 0

The A value is the same, so we leave the markings.

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

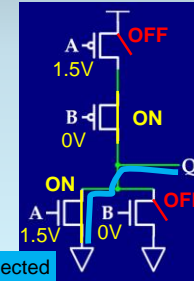

Q connected to 0V

ECE 120: Introduction to Computing


© 2016 Steven S. Lumetta. All rights reserved.

slide 26


It's a NOR Gate!

We see that $Q = (A+B)'$.

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

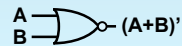

NOR gate

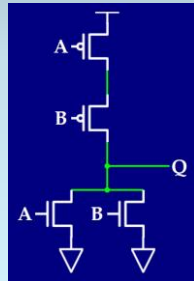

Q connected to Vdd

ECE 120: Introduction to Computing


© 2016 Steven S. Lumetta. All rights reserved.

slide 27

And Just One More to Analyze...

What if A=0?

A	B	Q
0	0	1
0	1	1
1	0	0
1	1	0

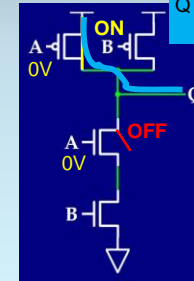

ECE 120: Introduction to Computing


© 2016 Steven S. Lumetta. All rights reserved.

slide 28

Notice that the Circuit is Symmetric in A and B

What if B=0?

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	1

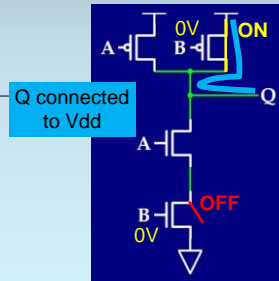


ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 29

And if Both A = 1 and B = 1?

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

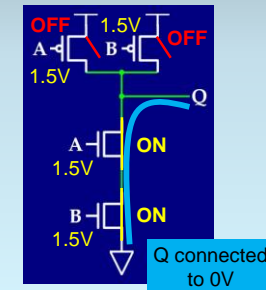

ECE 120: Introduction to Computing


© 2016 Steven S. Lumetta. All rights reserved.

slide 30


It's a NAND Gate!

We see that $Q = (AB)'$.

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

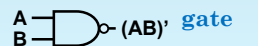

NAND
gate

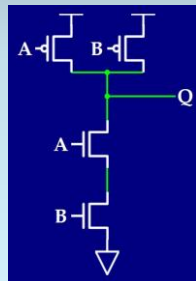

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 31

Generalizing to More Inputs

Notice the common features

- p-type always connected to Vdd.
- n-type always connected to 0V.
- One side is parallel, the other is serial (they are duals* of one another).

Can you generalize NAND/NOR to more inputs?

Let's try it in the online tool...

*See Notes Section 2.2.1.

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 32

A Couple of Practical Limits

Gates scale to about 4 inputs before using more gates is a better approach.

One can easily

- design an AND or an OR gate with CMOS
- by swapping n-type with p-type,
- but MOSFETs don't work properly in those designs.
- Try it in the online tool to see what happens.
- (NAND followed by NOT is, of course, AND.)