

University of Illinois at Urbana-Champaign  
Dept. of Electrical and Computer Engineering

## ECE 120: Introduction to Computing

### Example of Serialization

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 1

## Review of General Bit-Slice Model

### General model parameters


**N-bit** operands

**P** bits of input from operands

**Q** bits of output produced

**M** bits between bit slices

**R** bits of final output (not shown; produced by output logic operating on **M** bits from last bit slice).

 

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 2

## N-bit Bit-Slice Comparator

### Comparator parameters


**N-bit** operands  $A_{N-1}A_{N-2}...A_1A_0$  and  $B_{N-1}B_{N-2}...B_1B_0$

**P = 2**

**Q = 0**

**M = 2**

**R = 2**

 

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 3

## Parameter Values for a Serial Comparator

### Comparator parameters


**N-bit** operands

**P = 2**

**Q = 0**

**M = 2**

**R = 2**

 

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 4

## Initialization of a Serial Comparator


Our comparator bit slice uses the representation shown here to pass information between slices.

What values should be passed to the first bit slice?

$A = B$ , so  $C_1 C_0 = 00$

$C_1$	$C_0$	meaning
0	0	$A = B$
0	1	$A < B$
1	0	$A > B$
1	1	not used

## Example: A Serial Comparator

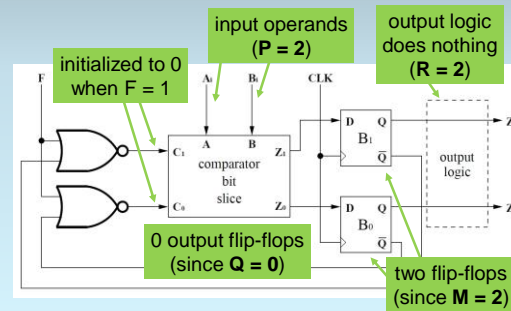

## Discrete Time Implies Delayed Results: $N = 4$

cycle #	F	A	B	$B_1$	$B_0$	$C_1$	$C_0$	$Z_1$	$Z_0$
0	1	0	1	bits	bits	0	0	0	1
1	0	1	1	0	1	0	1	0	1
2	0	1	0	0	1	0	1	1	0
3	0	0	1	1	0	1	0	0	1
4	x	x	x	0	1	0	?	?	?

yellow = inputs

(green = bit slice labels)


blue = outputs

## A Serial Comparator Consists of Three Parts

Let's analyze the area of a serial comparator.


We have:

 - one bit slice,
- two flip-flops, and
- two 2-input NOR gates (selection logic).



## A Serial Comparator Contains One Bit Slice

Assume the smaller version of the bit slice.  
So we need **six 2-input NAND gates** and **two inverters**.

 

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 9

## A Serial Comparator Consists of Three Parts

Let's analyze the area of a serial comparator.

We have:

- one bit slice,
- two flip-flops, and
- two 2-input NOR gates (selection logic).

six 2-input NAND  
and two inverters

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.


slide 10

## A Serial Comparator Uses Two Flip-Flops

A flip-flop is two latches and an inverter.

If we use NOR gates for the first latch, we don't need the extra inverter.\*

 So **eight 2-input gates** and **two inverters** (each).



\*And real designs, optimized at the transistor level, are even smaller.

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 11

## A Serial Comparator Consists of Three Parts

Let's analyze the area of a serial comparator.

We have:

- one bit slice,
- two flip-flops, and
- two 2-input NOR gates (selection logic).

six 2-input NAND  
and two inverters

16 2-input gates  
and four inverters

Total:  $6+16+2 = 24$  **2-input gates** and  
 $2+4 = 6$  **inverters**.

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 12

## Serial Design is Smaller for $N \geq 4$

To handle **N-bit** operands, a bit-sliced design requires:

- **6N 2-input gates**, and
- **2N inverters**.

A serial design (independent of **N**) requires

- **24 2-input gates**, and
- **6 inverters**.

**The serial design is smaller for  $N \geq 4$ .**

## Serial Designs are Slower than Bit-Sliced Designs

The tradeoff? Serial designs are **slower** than bit-sliced designs.

### Why?

There are three reasons:

1. All paths matter.
2. Selection logic and flip-flops add to delay.
3. Other logic may further reduce the speed of the common clock.

Let's look at each in more detail.

## All Paths Matter in a Serial Design

In an **N-bit bit-sliced design**,

- All external inputs appear at time 0,
- So only the **slice-to-slice paths** in the bit slice **contribute to the multiplier on N**.
- **Other paths contribute only constant time** to the overall delay in the design.

In a **serial design**, all paths matter.

- All input bits arrive in the cycle in which they are consumed, so
- **long paths from any input can slow down the design** overall.

## Flip-Flops and Selection Logic Add to Delay

Flip-flops take time

- To store values,
- To produce values.

And the selection logic sits between the flip-flops and the bit-slice inputs.

The clock cycle

- must be long enough
- to account for all of these delays.

## Clock Speed is Determined by the Slowest Logic

The longest path through combinational logic determines the speed of the common clock.

In practice,

- engineers identify complex and/or important elements and
- work hard to make them fast or
- to split them into several cycles.

Even if a serial design's logic needs only 0.1 clock cycles, operating on **N-bit** operands still takes **N** clock cycles.

## Assume Four Gate Delays On Either Side of Clock Edge

Let's analyze the delay of a serial comparator.

We can count gate delays

- in the bit slice, and
- for the selection logic.


### What about the flip-flops?

Let's assume

- **four gate delays** of stable D input needed **before the rising edge**, and
- **four gate delays after the rising edge**.
 
## When Are Inputs Available?

A rising edge arrives at  $t = 0$  (gate delays).




## Delay Analysis for the Bit Slice

**A to Z<sub>i</sub>: 3 gate delays (ignoring NOT)**

**C<sub>1</sub> to Z<sub>i</sub>: 2 gate delays**


**B to Z<sub>i</sub>: 3 gate delays**

**Paid 4 gate delays for flip-flops.**

 

## When Are Results Stored?

A rising edge arrives at  $t = 0$  (gate delays).

 

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 21

## Serial Design is At Least 5.5x Slower

To handle **N-bit** operands, a bit-sliced design requires  **$2N + 1$  gate delays**.

For a serial design,

- the clock cycle must be **at least 11 gate delays**, and
- we must execute for **N** cycles, so
- N-bit** operands require **at least 11N gate delays**.

**The serial design is at least 5.5x slower.**

(And may be even slower!)

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 22

## Bit-Sliced and Serial Designs are Extrema

Both designs are **simple**.

Serial designs are relatively **small, but slow**.

Bit-sliced designs are **fast, but large**.

But we **can build anything in between**:

- 2 bit slices per cycle,
- 3 bit slices per cycle,
- and so forth.

And/or **optimize more than one bit slice**  
(increase complexity).

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 23

## An Example of Partial Serialization in Practice

In one generation of Intel processors,

- the designers included **16-bit adders**
- clocked at twice the main clock speed (**6 GHz** instead of **3 GHz**).

These adders could be used to ...

- perform a **single 32-bit add**  
(two cycles at 6 GHz), **or**
- perform **two 16-bit adds**  
for multimedia codes.

ECE 120: Introduction to Computing

© 2016 Steven S. Lumetta. All rights reserved.

slide 24